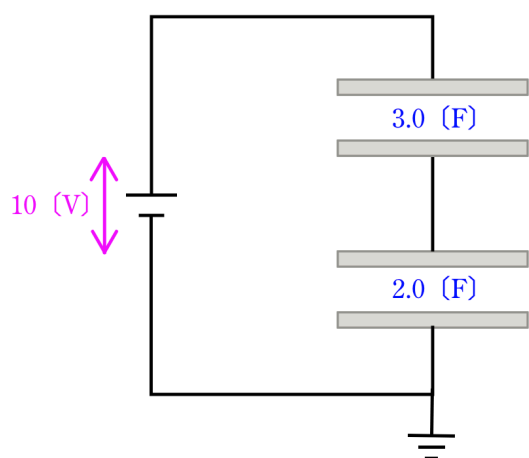


☆コンデンサーの接続（直）


数値を例に...

合成容量： C (F)


$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$



ひとまとめ...

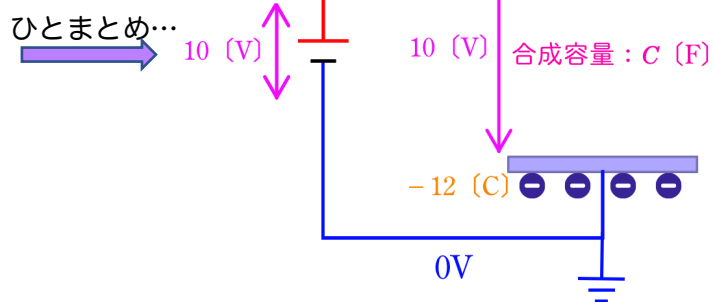

文字で...

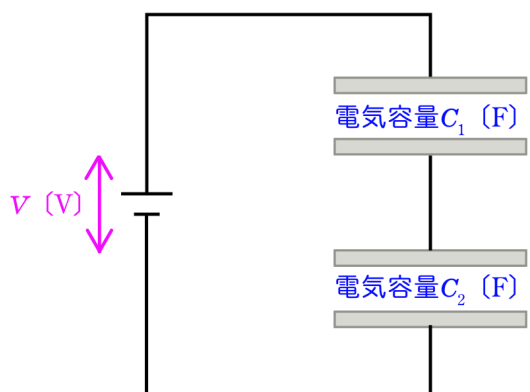

ひとまとめ...

