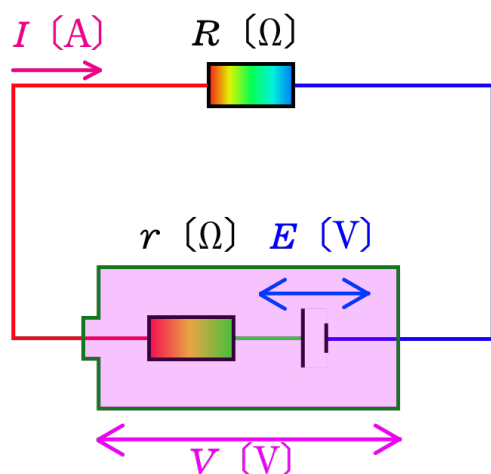


☆電池の起電力と内部抵抗



$$\begin{cases} V: \\ r: \\ E: \end{cases} \rightarrow V =$$

※起電力と内部抵抗を測定

$$\begin{cases} I=0.2 \text{ (A) のとき } V=1.5 \text{ (V)} \\ I=0.4 \text{ (A) のとき } V=1.4 \text{ (V)} \\ I=0.6 \text{ (A) のとき } V=1.3 \text{ (V)} \end{cases}$$

