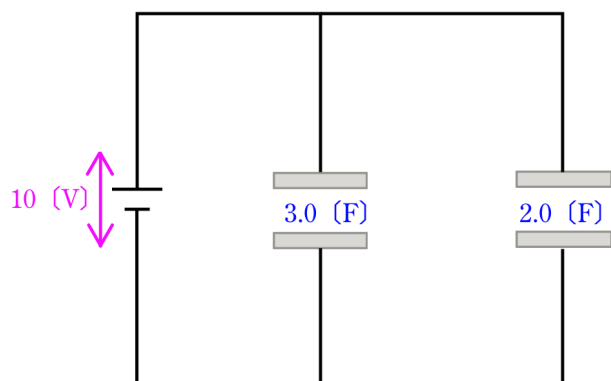



☆コンデンサーの接続（並列）

$$\text{合成容量} : C = C_1 + C_2 \text{ (F)}$$


数値を例に...



ひとまとめ...

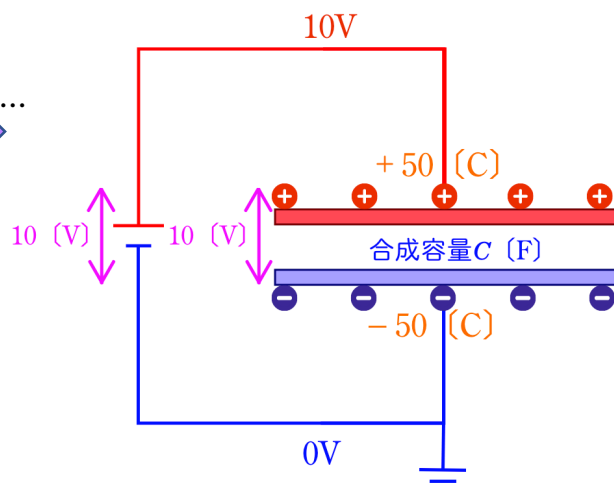

文字で...

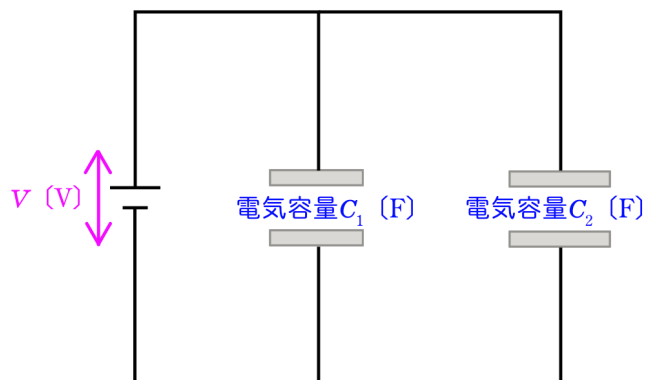

ひとまとめ...

